

# Delay Relevant Reliability of CMOS Logic Circuits in Near/Sub Threshold Region

Chen Jiaoyan, Christian Spagnol, Satish Kumar  
Supervisor: Dr. Emanuel Popovici  
University College Cork

# Possible Reliability Model

- What is **Reliability**?

**Permanent** errors: failure to switch from 0-1 / 1-0.

**Performance**, i.e. speed/delay: The **higher** the speed is, the **lower** the reliability might be.

- How to link the **delay** to **Reliability**?

$$R(d, f) = 1 - P(d > \frac{1}{f})$$

*d = delay; f = reference frequency; P = Probability*

# How to Get the Reliability Model

- VDD @ Near/Sub threshold region ( $<0.4V$ ), Models: Inverter, AND
- 45nm process, hspice (monte carlo) simulation: 10,000 samples
- Variation to concern: VDD, process variation, temperature

**VDD:** @0.3V with 50mV variation (gauss distribution, sigma =1)



**Process Variation:**  $V_{thn}=0.32V$ ,  $V_{thp}= -0.3V$  with 50mV variation (gauss distribution, sigma =3), plus 10% variation for thickness of the oxide.

**Assumption:** Input follows the change of VDD.

- Temperature has little impact on delay compared with other two.

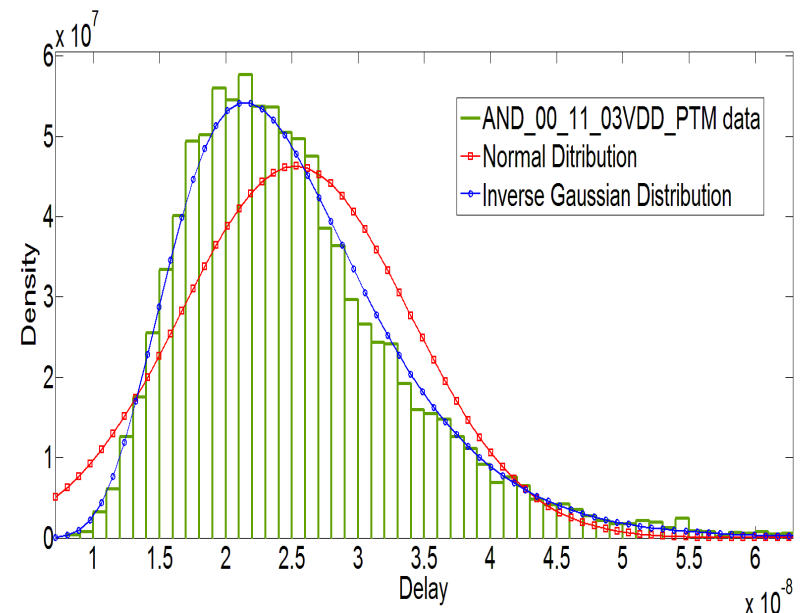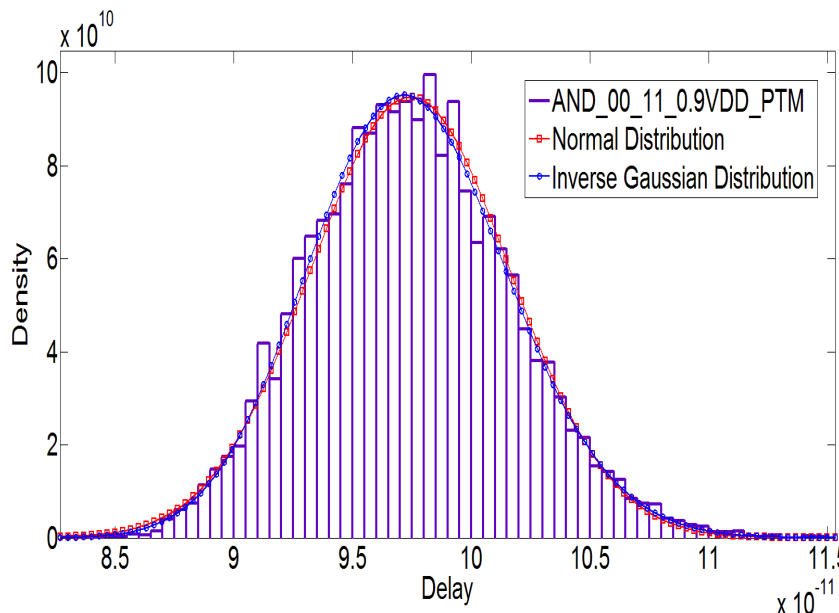
# Related Work

- In [1], with similar aspects of variation, it claimed that **Normal (Gaussian)** approximation matched the Probability Density Functions (PDFs) of the propagation delays.
- However, **No** strong theoretical proof for this approximation. So is it **true?**
- PTM (predictive model) AND gate input switch from 00-11 @ **0.9VDD**, **0.3VDD** with process variation.


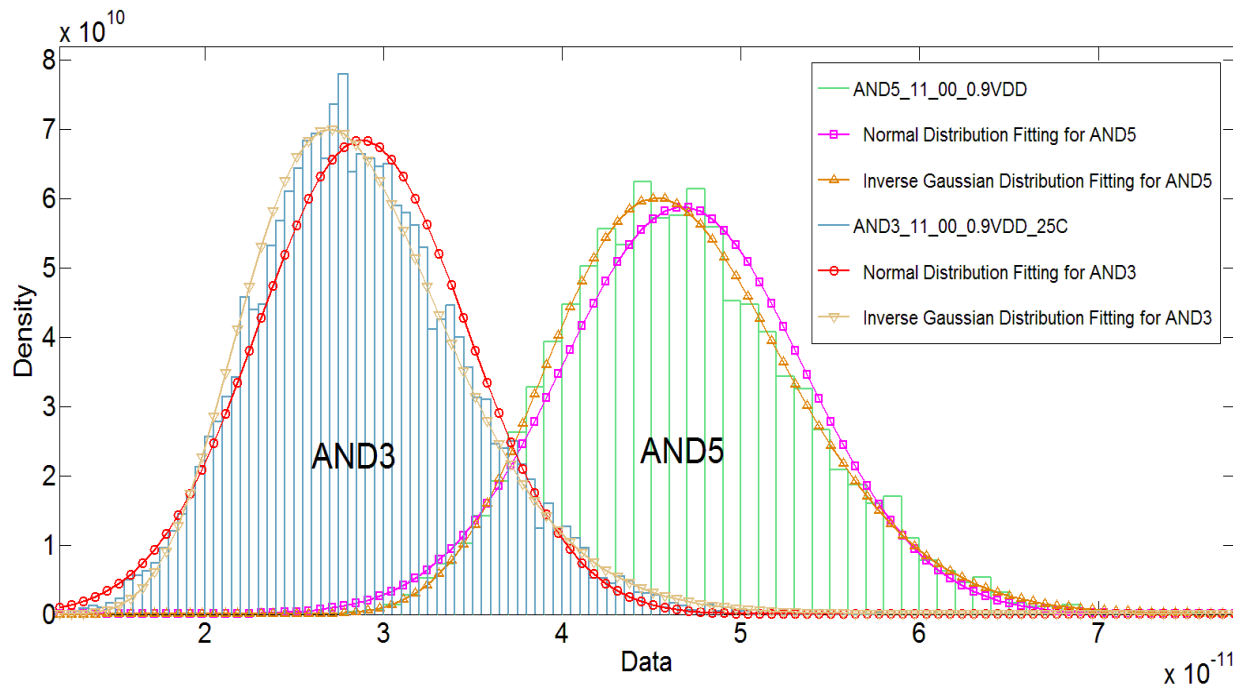
# Further Validation

- Five cascaded AND gates suffer both **process** variation and **power supply** variation @ 0.9V.
- Only the third and fifth AND gates are shown for the clarity.
- Again, Inverse Guassian fitting **beats** the normal distribution.



# Normal or Inver Gaussian & Why?

- **Normal (Gaussian)** distribution: a number falling between **any two real numbers**. Consider the negative delay, possible? Plus, it is **symmetric**.


**Versus**

- **Inverse Gaussian** distribution: a **Brownian Motion** with **positive** drift takes to reach a fixed positive level (the movement of electron).
- **Brownian Motion**: an idealised approximation to actual random physical processes with **finite** time scale.

**Any doubt?** Yes, is it because guassian distribution is used in those variations?  
Let's try something else.
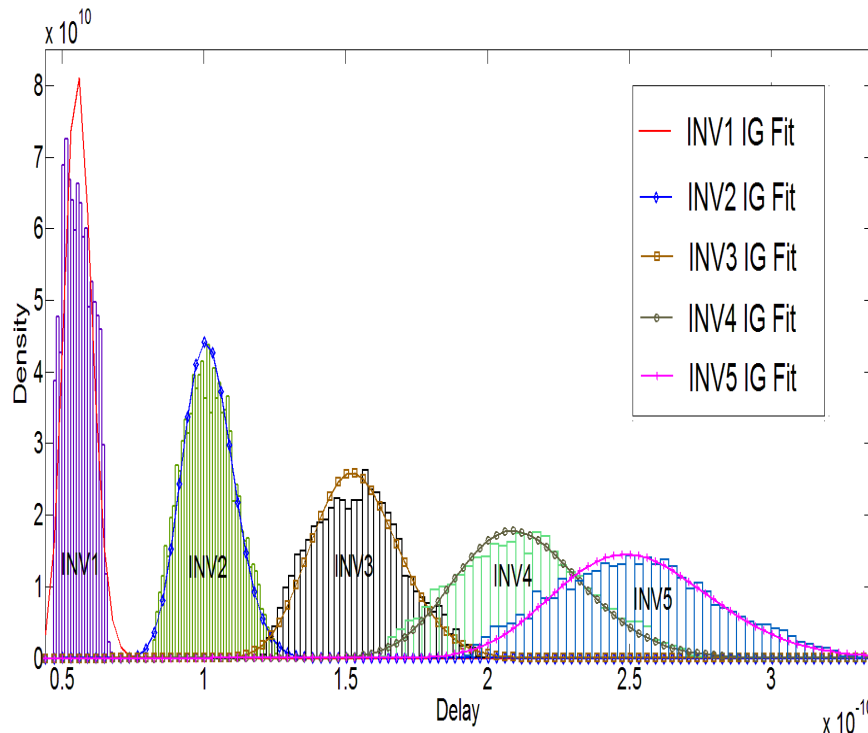
# Inverse Gaussian valid for Uniform distribution?


- We built a chain of five inverters where **uniform** distribution was used for the **V<sub>th</sub>** variation,  $V_{DD}=0.3V$ .



After 1st stage, the delay fitted again to the inverse Gaussian distribution.
 
# How to take advantage of Inverse Gaussian Dis.?

- A chain of **seven** Inverters was simulated with both **VDD** and **process** variations. So how will the PDFs propagate?



There are **two** parameters for Inverse Gaussian Distribution:  $\mu$  is the mean parameter;  $\lambda$  is the shape parameter.

$$f(x; \mu, \lambda) = \left[ \frac{\lambda}{2\pi x^3} \right]^{1/2} \exp \frac{-\lambda(x - \mu)^2}{2\mu^2 x}$$


**Scaling:**

$$X \sim IG(\mu, \lambda) \Rightarrow tX \sim IG(t\mu, t\lambda).$$



# How good is scaling?

	Input Switch	$\mu$ ( $e^{-10}$ )	$\Delta\mu(e^{-10})$	$\lambda$ ( $e^{-10}$ )	$\Delta\lambda(e^{-10})$
INV1	1-o(charging)	0.65	/	0.37	/
INV2	0-1(discharging)	1.3	0.65	2.6	2.23
INV3	1-o(charging)	2.3	1	2.4	-0.2
INV4	0-1(discharging)	3.0	0.7	4.5	2.1
INV5	1-o(charging)	4.0	1	4.8	0.3
INV6	0-1(discharging)	4.7	0.7	6.4	1.6
INV7	1-o(charging)	5.5	0.8	6.6	0.2
Average (charging)		/	0.9	/	0.1
Average (discharging)		/	0.7	/	2.0

 


- The increment of  $\mu$  is quite steady (blue line), that of  $\lambda$  increase like stair-wise (green line) which is due to the characteristic of NMOS and PMOS (discharging and charging).

# Is it the same for AND gate?


- A chain of **five** AND gates was simulated with both **VDD** and **process** variations.
- Four different events (input switching) were considered:  
**10-11**, **11-01**, **00-11**, **11-00** (where we regard 10 and 01 are the same)

**10-11**

 


# Is it same for AND gate?


10-11 (output 0-1)

 


00-11 (output 0-1)

 

11-01 (output 1-0)

 

11-00 (output 1-0)

 

- $\mu$  (blue line) and  $\lambda$  (green line) increase almost linearly while the increment is different for different cases which is due to charging and discharging (PMOS and NMOS).

10-11	$\mu (e^{-10})$	$\Delta\mu(e^{-10})$	$\lambda (e^{-10})$	$\Delta\lambda(e^{-10})$
AND <sub>1</sub>	2.3	/	3.4	/
AND <sub>2</sub>	4.4	2.1	5.9	2.5
AND <sub>3</sub>	6.5	2.1	8.4	2.5
AND <sub>4</sub>	8.7	2.2	10.8	2.4
AND <sub>5</sub>	10.6	1.9	13.3	2.5
Average	/	2.1	/	2.5

00-11	$\mu (e^{-10})$	$\Delta\mu(e^{-10})$	$\lambda (e^{-10})$	$\Delta\lambda(e^{-10})$
AND <sub>1</sub>	2.6	/	3.8	/
AND <sub>2</sub>	5.6	3.0	7.3	3.5
AND <sub>3</sub>	8.6	3.0	10.8	3.5
AND <sub>4</sub>	11.7	3.1	14.2	3.4
AND <sub>5</sub>	14.3	2.6	17.6	3.4
Average	/	2.9	/	3.5

11-01	$\mu (e^{-10})$	$\Delta\mu(e^{-10})$	$\lambda (e^{-10})$	$\Delta\lambda(e^{-10})$
AND <sub>1</sub>	1.9	/	3.4	/
AND <sub>2</sub>	4.4	2.5	5.3	1.9
AND <sub>3</sub>	6.3	1.9	8.2	2.9
AND <sub>4</sub>	8.4	2.2	10.6	2.4
AND <sub>5</sub>	10.6	2.2	12.9	2.3
Average	/	2.2	/	2.4


11-00	$\mu (e^{-10})$	$\Delta\mu(e^{-10})$	$\lambda (e^{-10})$	$\Delta\lambda(e^{-10})$
AND <sub>1</sub>	1.5	/	3.1	/
AND <sub>2</sub>	3.7	2.2	5.4	2.3
AND <sub>3</sub>	5.9	2.2	7.8	2.4
AND <sub>4</sub>	8.2	2.3	10.3	2.5
AND <sub>5</sub>	10.2	2.0	12.3	2.0
Average	/	2.2	/	2.3

# What can we learn?

- We may propagate the PDFs by adding  $\mu$  and  $\lambda$  respectively.
- So far, we considered the circuits with one type of gate only.  
So how about using INV and AND to build some circuits?  
i.e. Majority Voter, XOR gate
- Next step, running monte carlo simulation for two above mentioned gate and then to compare with the statistical estimation results (based on inverse Gaussian approximation) in the form of Cumulative distribution function (CDF).

 
# Majority Voter

- First, we can get specific  $\mu$  and  $\lambda$  of every individual cases for both AND and INV.
- And-Inverter** Graph (AIG) is used to generate the 3-bit Majority Voter, which gives the **output** as **1** when **more than one input** is **1**.




- **a, b, c** are inputs; **z** is output.
- **Dotted** line represents a **inverter**.
- **Solid** line is just a wire.

# Majority Voter – Comparison (CDF)

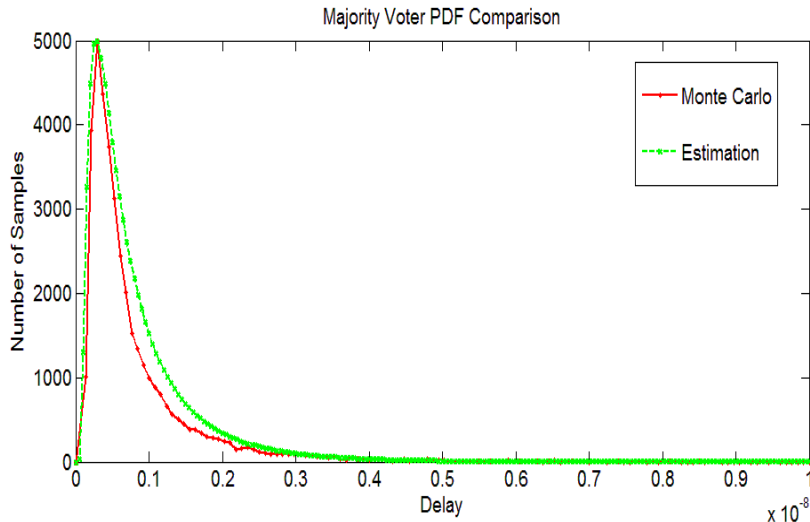

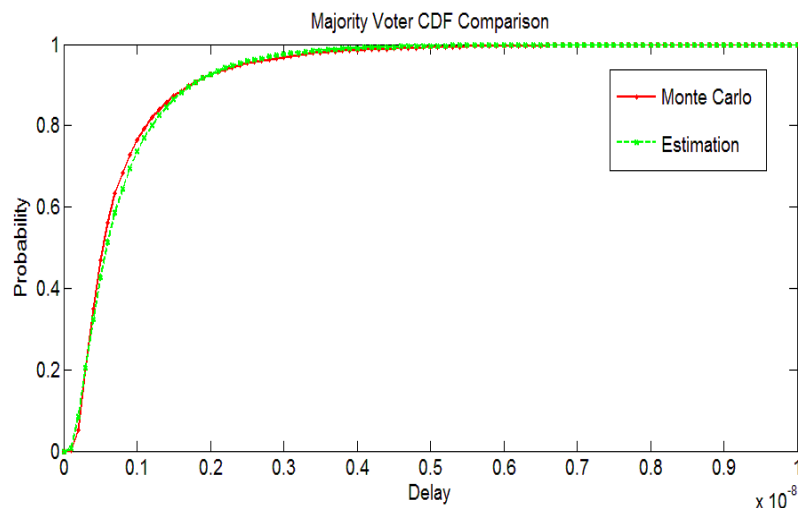
- We considered the **longest** path in the Majority Voter (3 ANDs, 2 INVs, 22 transistors).
- **Red** curve stands for Monte Carlo simulation results.
- **Green** curve stands for statistical approximation.
- Two sets of results are very **close** within **0.8%** average error.



Deviation	1ns	3ns	5ns	7ns	9ns	Average (0-10ns)
Majority Voter	3%	1%	0.3%	0.1%	0%	0.8%
 
# XOR Gate


- **And-Inverter** Graph (AIG) is used to generate the 3-bit XOR gate, which gives the **output** as **1** when there are **odd** number of **1's** at the inputs.




- **a, b, c** are inputs; **z** is output.
- **Dotted** line represents an **inverter**.
- **Solid** line is just a wire.



# XOR Gate– Comparison (CDF)

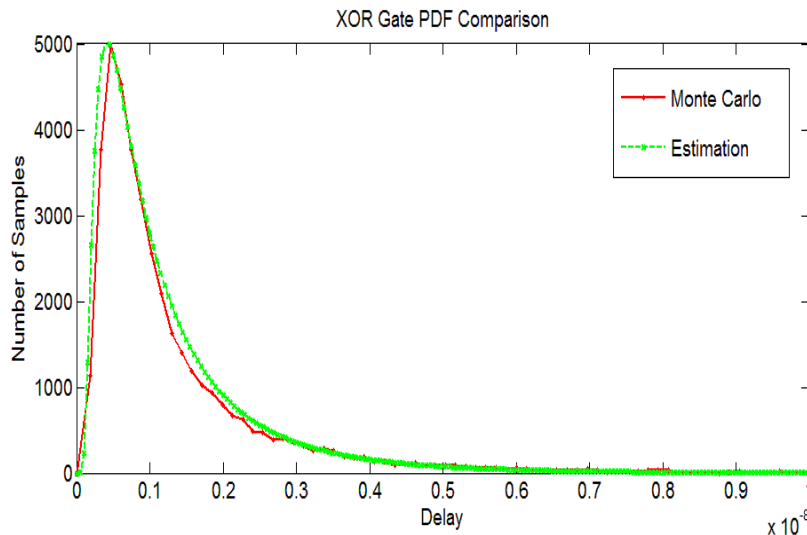

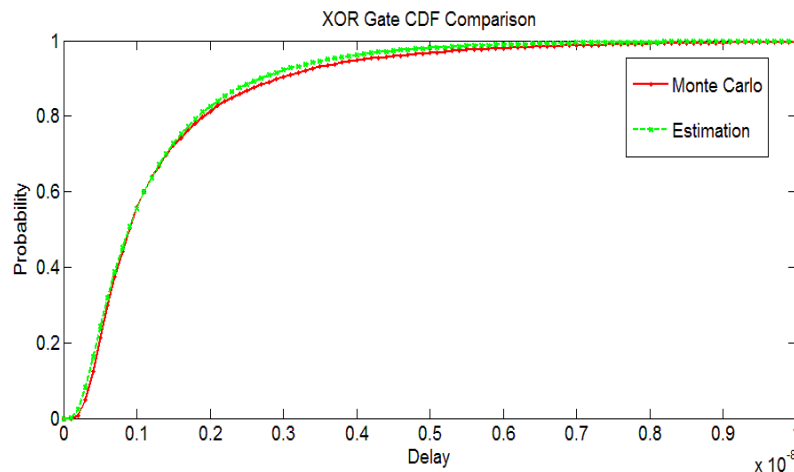- We considered the **longest** path in the XOR gate (4 ANDs and 5 INVs, 34 transistors).
- **Red** curve stands for Monte Carlo simulation results.
- **Green** curve stands for statistical approximation.
- Two sets of results are very **close** within **1.2%** average error.



Deviation	1ns	3ns	5ns	7ns	9ns	Average (0-10ns)
XOR	0.2%	2%	1.4%	0.7%	0.4%	1.2%

# Summary

- **Inverse Gaussian (IG)** was fitted to the propagation delay, which make more sense than Normal (Gaussian) distribution.
- AND, Inverter were explored and tested. **Scaling** of IG was demonstrated.
- **Majority Voter** and **XOR** were built using AIG.
- The longest path of each circuit was chosen. **Monte Carlo simulation** vs **statistical estimation** was carried on.
- The comparison of **PDF, CDF** graphs were exhibited to show the **high** accuracy of **IG** approximation.

# Acknowledgement

---

- This work has been sponsored by the European Commission FP7 FET-Open **iRISC** (Innovative Reliable Chip Designs from Unreliable Components) project.
- Also, I would like to thank **Science Foundation Ireland** (SFI).